



National Taiwan University



Memory Testing



Jiun-Lang Huang
ICDA/GIEE, NTU




- Overview
- Design and test considerations
- Memory testing
- Memory self test

A Simple Memory Block Diagram



Our focus is:
embedded memory.

 

Memory Testing Complexities




- Increasing density (the Moore's law).
 - More to test, more test time.
- Addition of logic to memories.
 - Random logic or memory testing techniques alone do not achieve high fault coverage for both.
- Memories are more deeply embedded.
 - 40 different memory designs on a single chip!!
 - Direct access is simply impossible.

Memory Testing Complexities - cont'd



- Increasing number of memory types.
 - Volatile: DRAM, SRAM, CAM, TCAM, ...
 - Multi-port, pseudo multi-port.
 - Non-volatile: Flash, EEPROM, FeRAM, MRAM, OUM.
- Different process technologies.
 - CMOS, SOI, SiGe, ...
 - Strained silicon, silicon on nothing, ...
- Redundancy
 - To enhance yield for large memories.
 - Involves locating the faults and allocating the redundant elements.

High Bandwidth Memory (HBM)

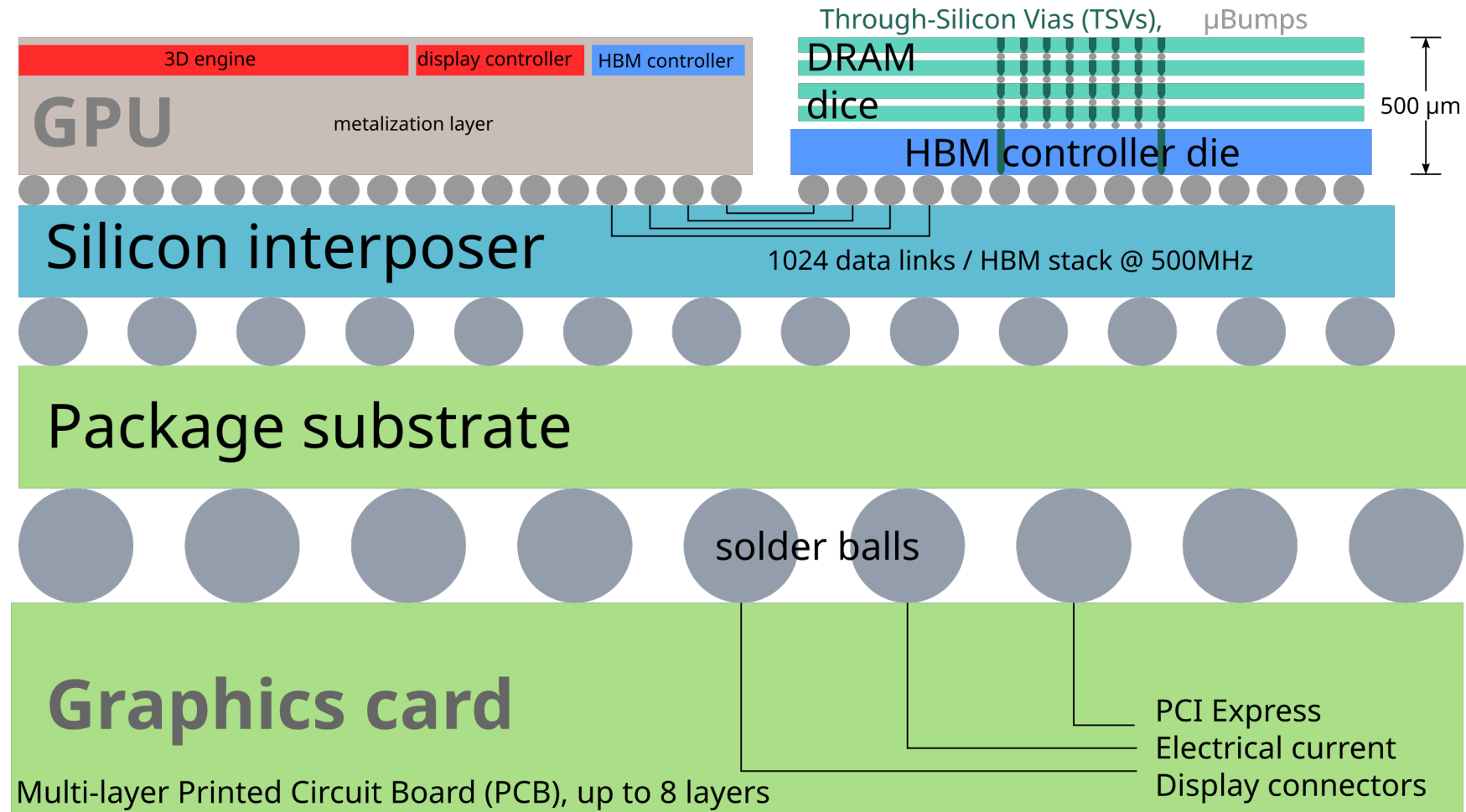


https://commons.wikimedia.org/wiki/File:High_Bandwidth_Memory_schematic.svg

NVIDIA Blackwell



New Class of AI Superchip

 The Two Largest Dies Possible—Unified as One GPU



<http://www.nextplatform.com/wp-content/uploads/2024/03/nvidia-blackwell-specs.jpg>

To BIST or Not?




- For embedded memories, BIST is the only practical solution.
 - Difficulties in accessing deeply embedded memories.
 - Need of at-speed testing.
 - Reducing test time.
 - Detecting subtle errors.
 - Better quality test.
 - Practically impossible w/ external testers.
 - Pushes the test into the design phase.
 - Better test re-use at each step in the manufacturing and use process.

Importance of Test Quality



 
- A defective memory can pass a poor quality test.
 - A memory that passes test is only as good as the test applied!
- Ignorance, i.e., testing without knowledge, may result in an artificially high yield but the result will be disastrous.



- Overview
- Design and test considerations
 - SRAM
 - Multi-port memories
 - DRAM
- Memory testing
- Memory self test



 - The mainstream of embedded memories.
 - Highest speed.
 - Can be designed for low power application requirements.
 - The easiest to use.




- SRAM cell design
- Read data path
- Write driver circuit
- Decoder circuitry
- Layout considerations
- Redundancy

A 6-T SRAM Cell



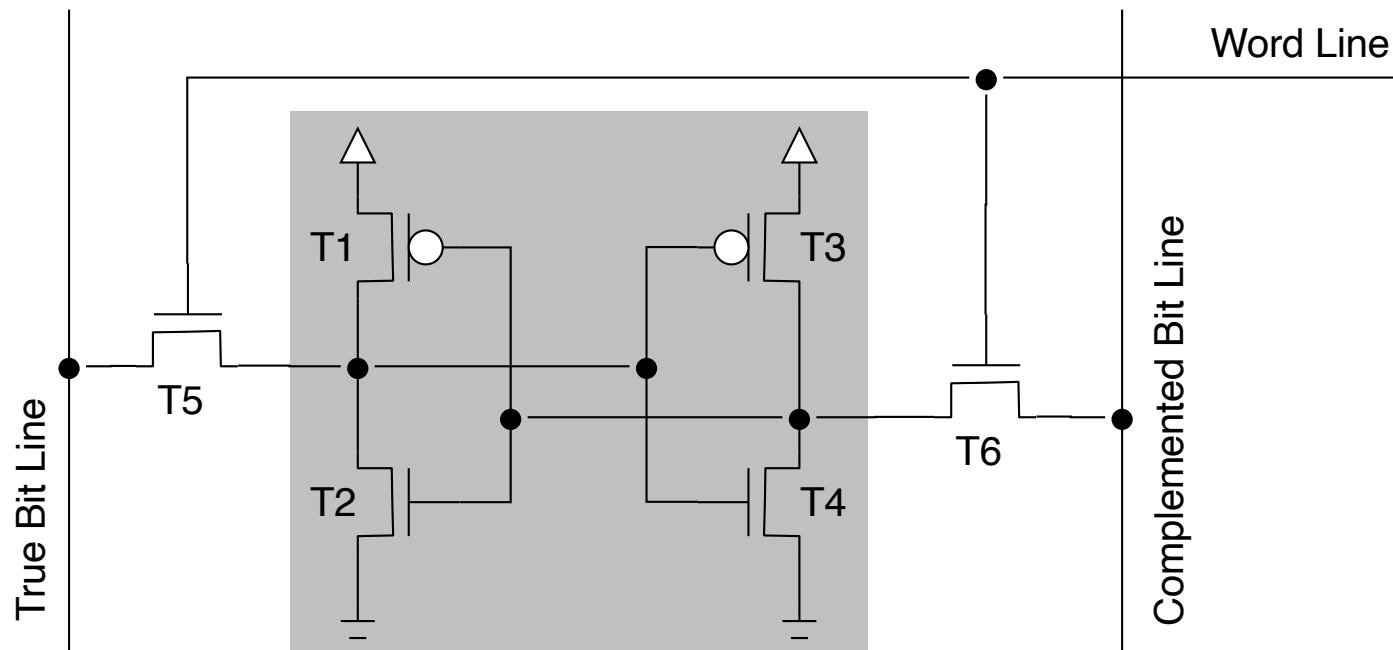- T1 and T3: pull-up devices.
 - Replaced by resistors in 4-T cells.
- T2 and T4: pull-down devices.
- T5 and T6: transfer devices.





Cell Stability - the Beta Ratio



- The ratio of the strength of the pull-down transistor divided by the strength of the transfer transistor.
 - Aka the “beta ratio.”
 - $\beta = (W_{\text{eff_pd}}/L_{\text{eff_pd}})/(W_{\text{eff_tfr}}/L_{\text{eff_tfr}})$
- A beta ratio of 1.5 to 2.0 is typical.
 - A beta ratio below 1.0 indicates that each time the cell is read, it is disturbed as well.
 - A defect-free SRAM cell must have a non-destructive read operation.


6-T Cell Layout

  

- Area is the major concern.
- The same defect mechanism causes different fault effects.




 - The same defect mechanism may cause different faults.
 - A resistive ground causes imbalance in the single ground contact layout.
 - A defective shared V_{dd} contact will fail a group of cells.
- Different fault models and test patterns should be used for different layout designs.





- SRAM cell design
- **Read data path**
- Write driver circuit
- Decoder circuitry
- Layout considerations
- Redundancy

Read Data Path

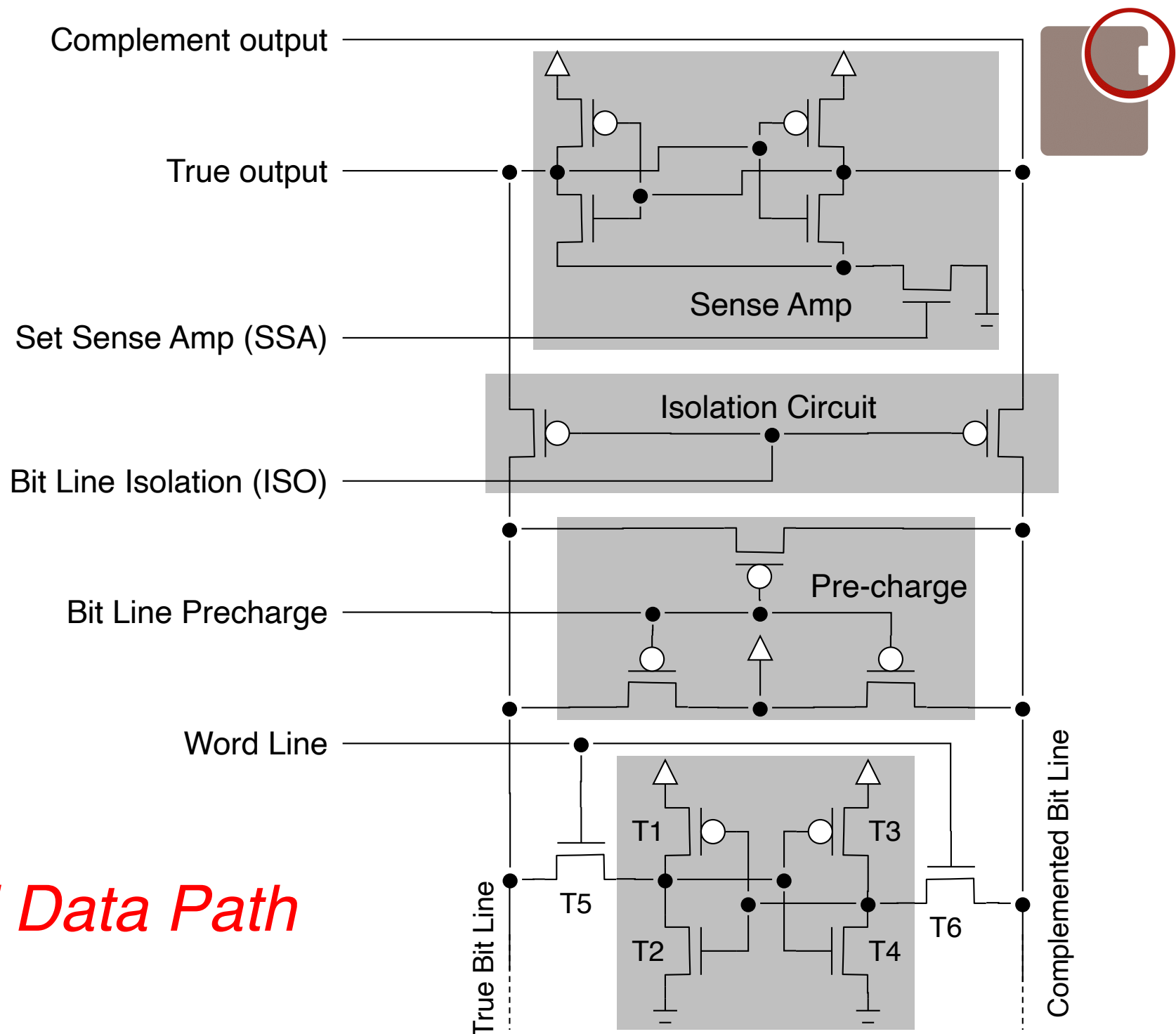


Bit Lines

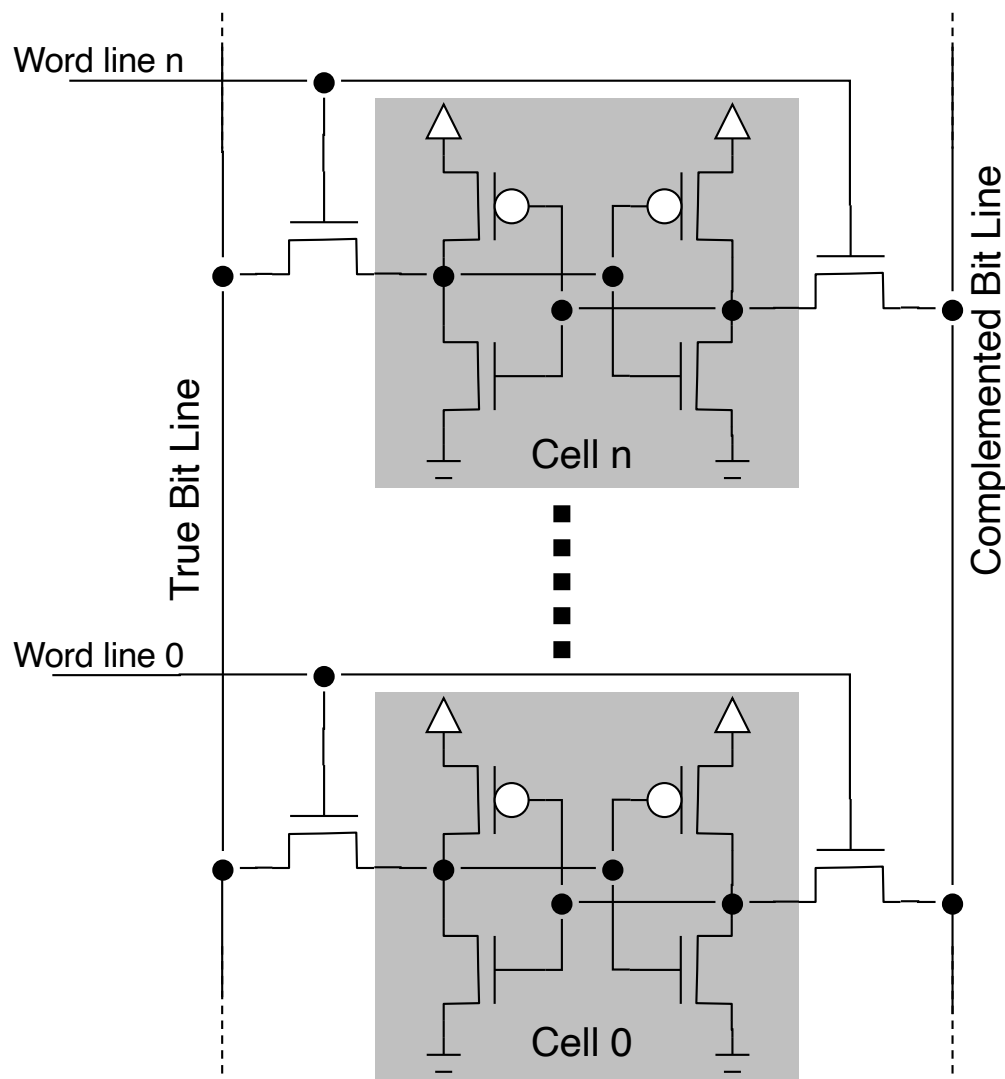 


- Cells are joined along a column by bit lines.
- High speed SRAMs always use a pair of bit lines for reading and writing.
 - On a read operation, the bit lines only swing a small amount.
- n is normally large, often being 256, 512, or 1024 in value.

Bit Lines - Read Operation

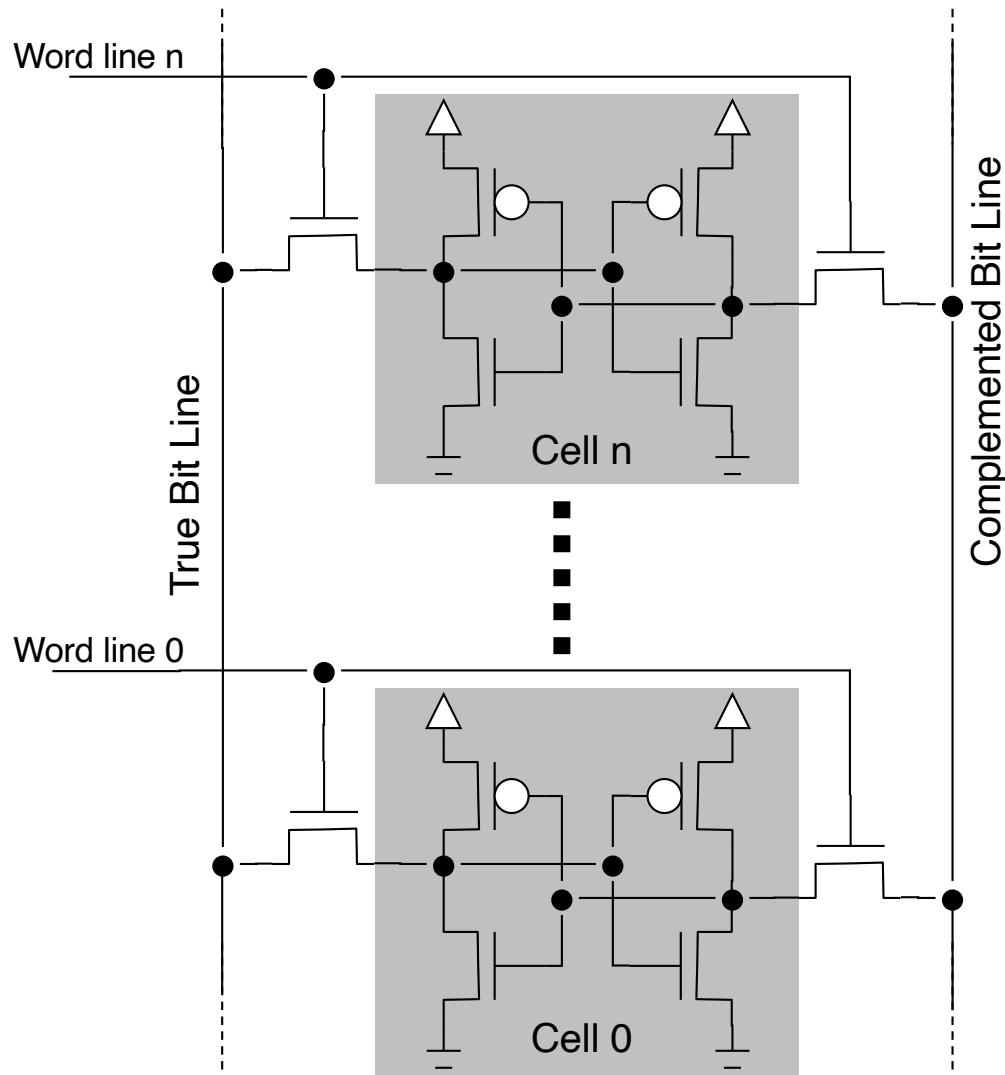


- Normally, the bit lines are pre-charged to V_{dd} .
- The word line corresponding to the address will go high and turn on the transfer devices.
- One of the bit lines will be pulled down.
 - The other remains unchanged.
 - The difference between the pair may only be 100 mV.

Pre-Charge

 


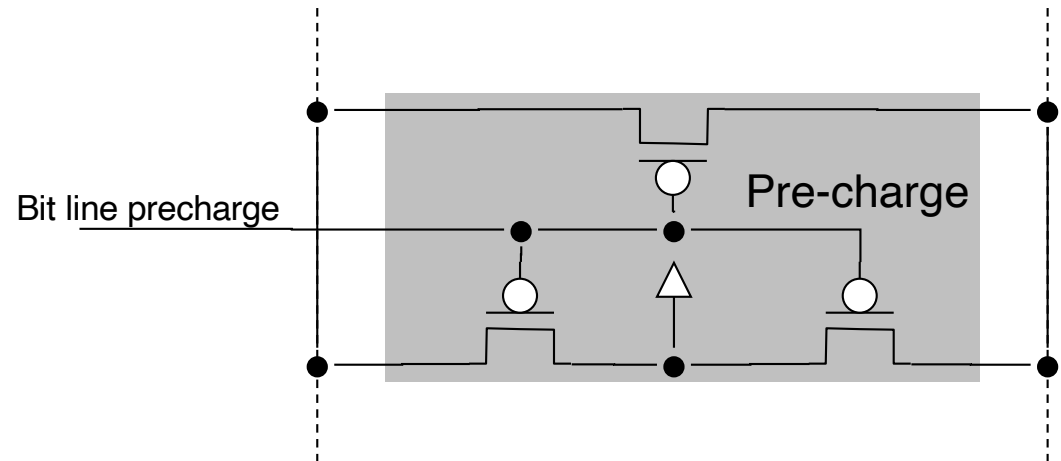- Pre-charging to V_{dd} is easier and the norm in SRAM designs today.
- During a read operation, the pre-charge circuit is normally turned off for a column that's being read.
- The pre-charge is often left on for the columns that are not being read.
 - Half-select state: pre-charge on and word line high.



Isolation Circuitry

- During a read operation, the bit lines are isolated from the sense amplifier once sufficient signal is developed.
- The purpose is to isolate the sense amplifier from the bit line's load and thus speed up the sense amplifier circuit operation.
- A sense amp may be shared by several columns. In this case, the isolation circuit is replicated to form a multiplexer.

 


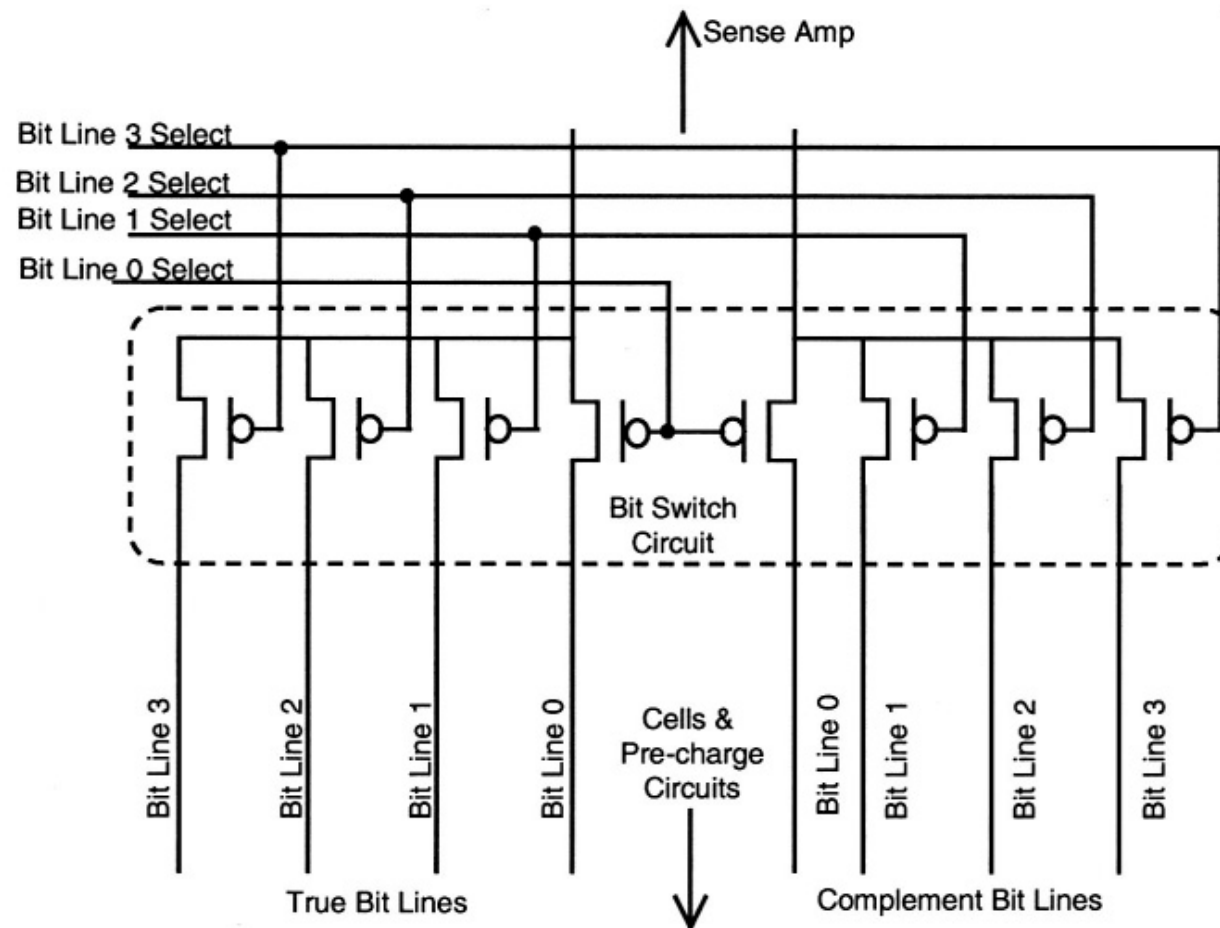


Figure 2-13. Bit switch isolation circuit.

Sense Amplifier

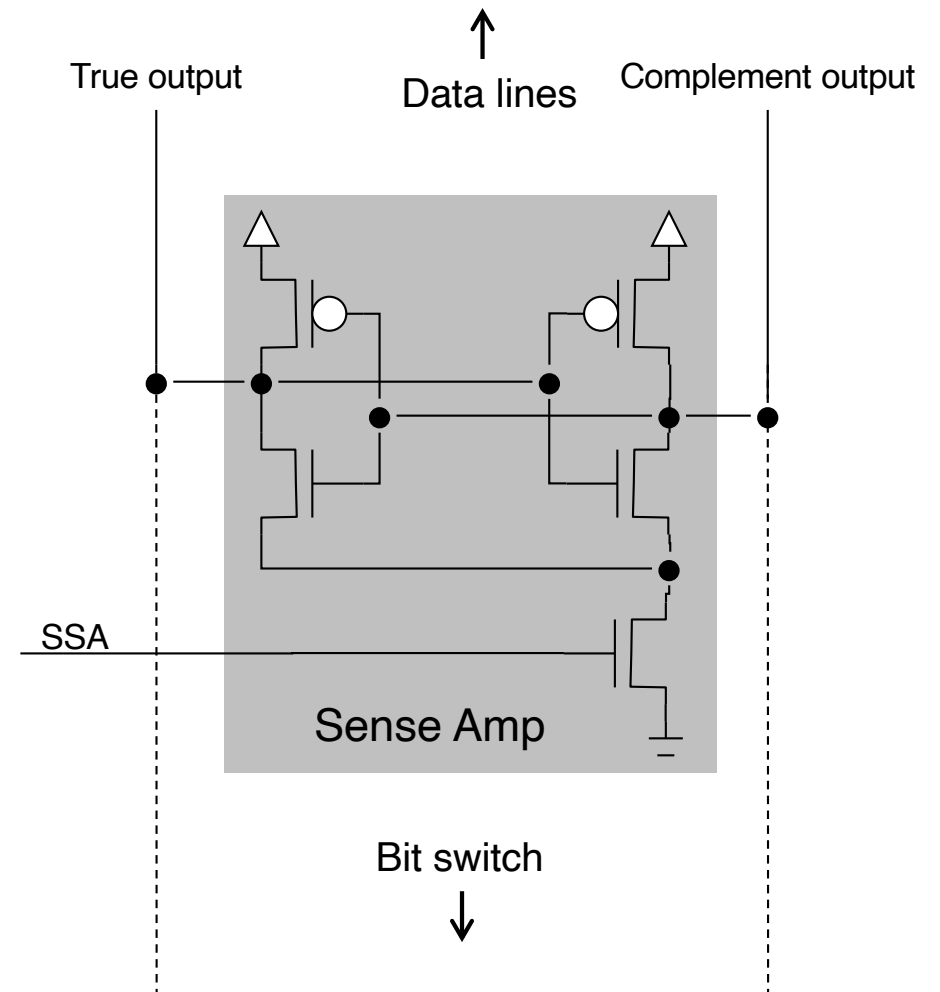

- Many types of sense circuitry. Shown here is a latch-type one.
- A second stage of sensing is often utilized to improve overall performance and latch the sensed result, regardless of the first stage's sense amp design style.



The ISO & SSA Control Signals




- ISO: bit line isolation
- SSA: set sense amp
- The timing relationship between the ISO and SSA signals is configuration dependent.
 - One sense amp per bit line pair: can use SSA to drive ISO.
 - Shared sense amp through the bit switch: SSA slightly before ISO.

The SSA Signal




- The timing of SSA is critical.
 - Too late: waste of time.
 - Too early: cause insufficient signal to reach the sense amp.
- The SSA delay must be very accurately modeled and designed robustly to track the bit line signal development.
 - In the existence of process, voltage, temperature variations.
 - Some solutions: dummy word line, dummy bit line, ...

An Example Read Timing (R0)

 


- In practice, ISO and SSA would be almost immediately adjacent in time.

Typical Read Timing

 



 - There are numerous subtle design variations in the designs of memory cells, isolation devices, bit switches, and sense amps.
- Different designs may necessitate or eliminate the need of some fault models.




- SRAM cell design
- Read data path
- **Write driver circuit**
- Decoder circuitry
- Layout considerations
- Redundancy


The Write Operation



- Writing a cell is accomplished by writing a “0” into either the true or the complement side of the cell and the cell latch causes the opposite side to go to a “1” state.
 - The NFET transfer devices can drive a strong “0” but do not drive a “1” very effectively.

Write Driver Circuit

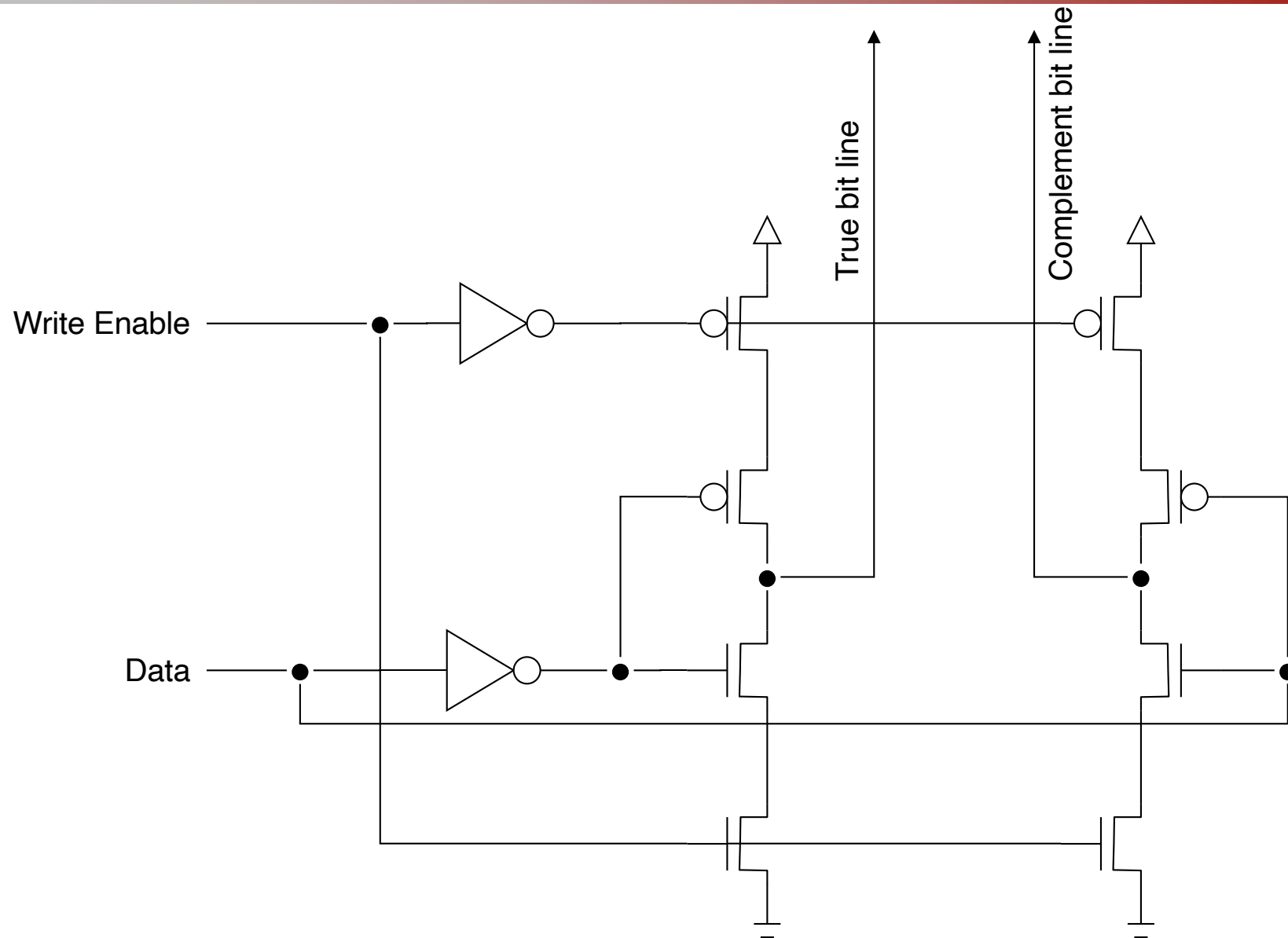

 


- SRAM cell design
- Read data path
- Write driver circuit
- **Decoder circuitry**
- Layout considerations
- Redundancy





- For larger memories, the address is divided into row, column, and even bank addresses.
 - Row: the y coordinate.
 - Column: the x coordinate.
 - Bank: sub-array, quadrant, or other terms.
- Different types of decoding circuitry may be employed for different addressing.

Example Static Decoder Circuitry

 


Example Dynamic Decoder Circuitry

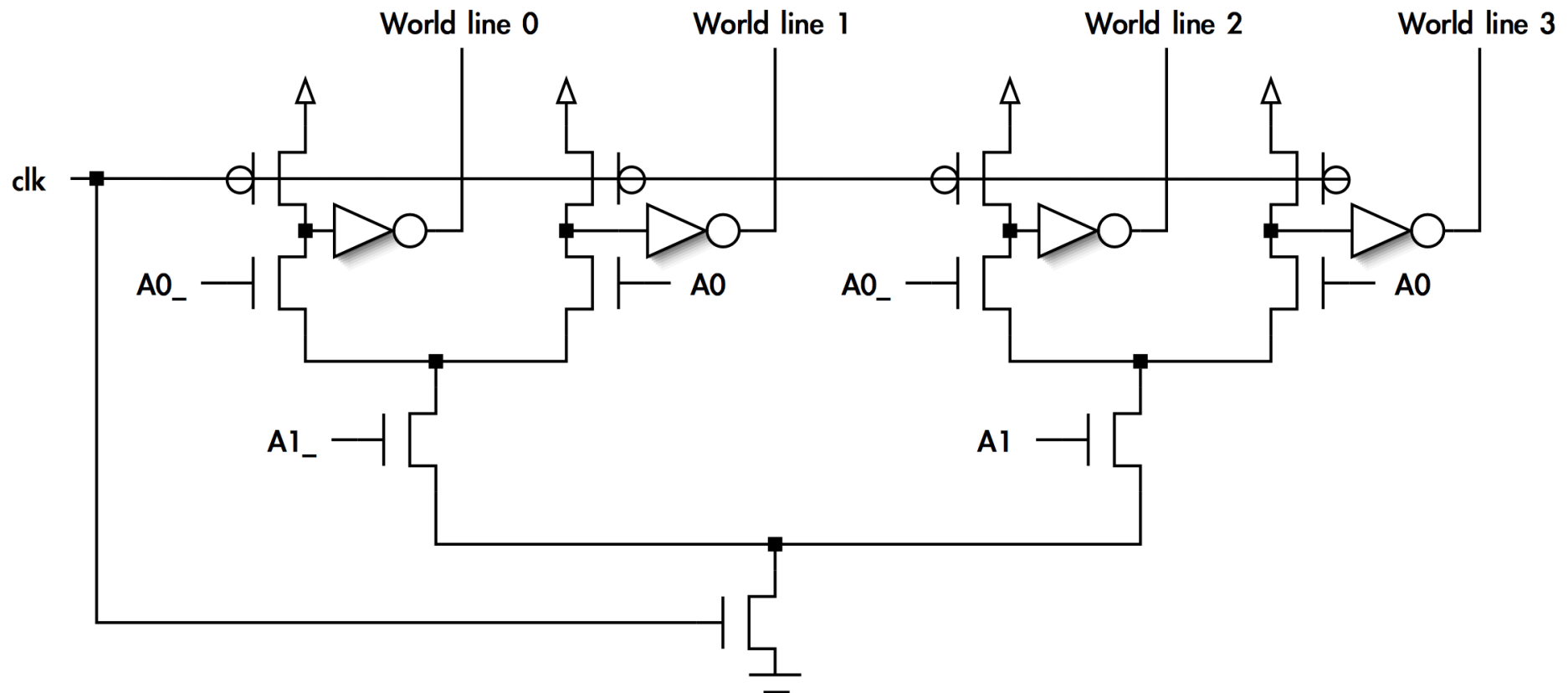


 


 - SRAM cell design
- Read data path
- Write driver circuit
- Decoder circuitry
- **Layout considerations**
- Redundancy




- Special attentions are paid to memory layout for various reasons:
 - Performing cell stepping, mirroring, and rotating to optimize overall memory size. (This can also be done in a sub-array basis.)
 - Spread bits of a single word in multiple sub-arrays for protection against soft errors.
 - Twisted bit lines to reduce capacitance coupling between adjacent bit lines.

Cell Stepping, Mirroring, and Rotating

  


Four stepped cells

 


Mirrored about the x-axis

More ...

 

Mirrored about the x-axis

 


Mirrored about the x and y-axis

Word Storage




- All of today's memories have more than a single I/O.
 - An address points to a “word,” not a single bit.
- Usually, the cells that store the bits from a single word are spread across multiple sub-arrays.
 - One of the reasons is protection against soft errors by reducing the possibility of two bits flip which cannot be detected by parity check.

Word Storage - cont'd

 


Entire word in a single sub-array

 


Word spreads across multiple sub-arrays

Bit Line Twisting

 


 - To reduce the capacitance coupling between long adjacent bit lines.
- Triple twist:
 - 1st pair twisted at half point.
 - 2nd pair twisted at 1 and 3 quarter points.
 - ...
- The triple twist configuration will force any coupling to be common mode which makes the sense amp less prone to erroneous evaluations.



- SRAM cell design
- Read data path
- Write driver circuit
- Decoder circuitry
- Layout considerations
- **Redundancy**

Redundancy

 

- Memories require redundancy to ensure that sufficient chip yield is obtained.
- A redundant element is a piece of memory that can replace a defective piece of memory.
 - In the form of spare rows, I/O, columns, blocks, or a combination of the above.
- The need for redundancy decreases on a per bit basis, but the total amount of redundancy needed is growing on a per chip basis.
- We will discuss this matter in later units.



- Overview
- Design and test considerations
 - SRAM
 - Multi-port memories
 - DRAM
- Memory testing
- Memory self test

Multi-Port Memories




- Allows more than one operation per cycle.
 - Useful when a designer would like to read data in each cycle and would also like to write data in each cycle.
- The number of multi-port memory applications will continue to grow as system engineers strive to increase performance and recognize the availability and utility of multi-port memories.

Multi-Port Memories




- **Cell basics**
- Timing issues
- Layout considerations



Block Diagram

 

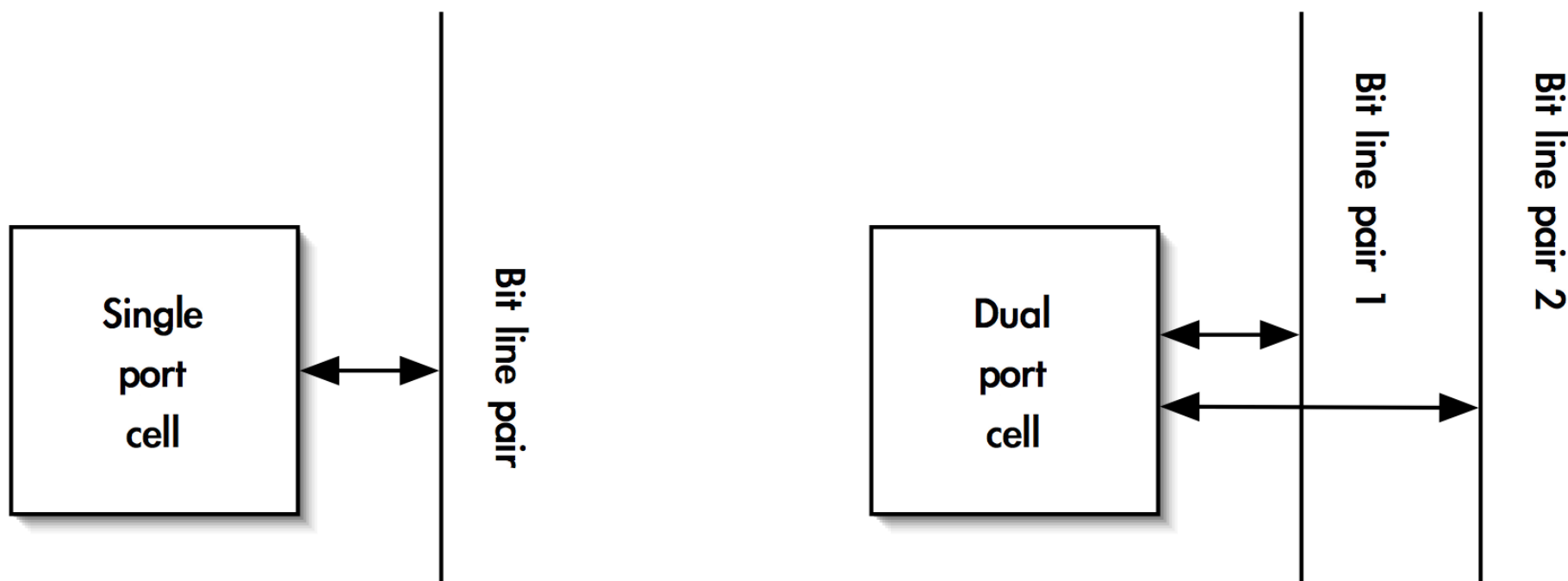- A multi-port memory cell has to have more than one access port.
- We assume multi-port SRAM here, although it is possible to have other types of multi-port memories.




A Simple Two-Port Cell

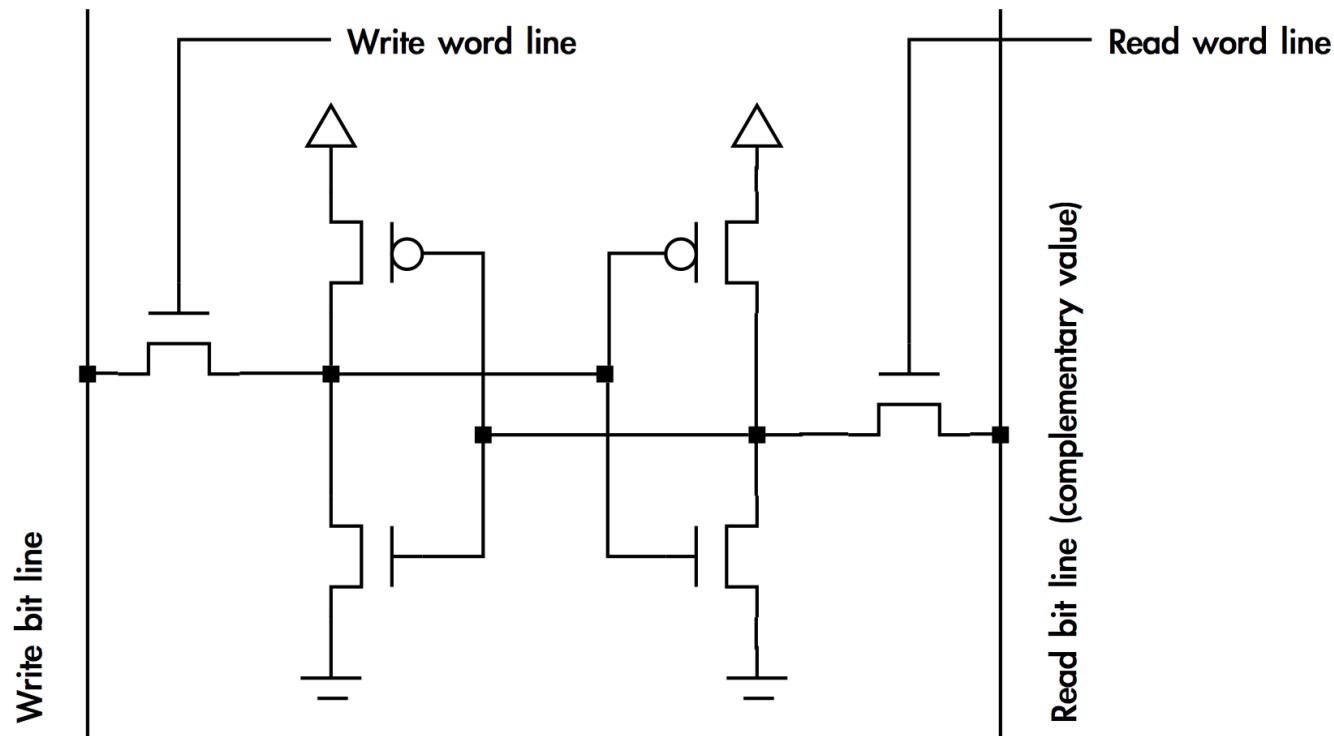 

- Single-ended read operation is slow.
 - Need larger voltage swing, but simple sensing scheme, e.g., an inverter.
- NFET is not very effective at writing 1.
- This topology should be avoided.

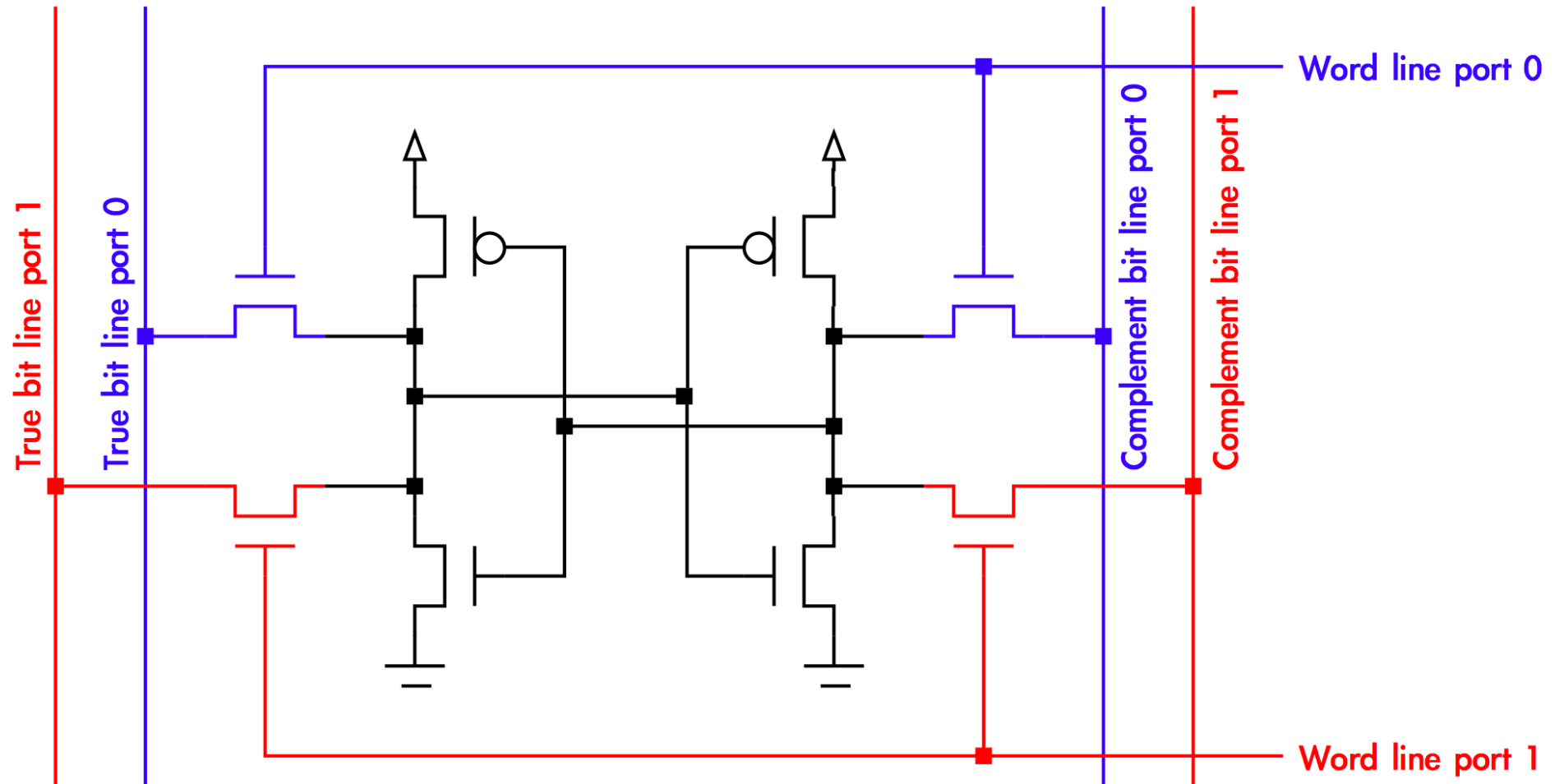The Eight-Device Two-Port Read/Write Cell



Stability of the Multi-Port Cell




- Much trickier than a one-port cell.
 - Simultaneous operations are performed regularly.
- The beta ratio for an n read port memory.

$$\beta = \frac{W_{PullDownFET} / L_{PullDownFET}}{\sum_{n=1}^{\#ReadPorts} \left(W_{TsfrFET_n} / L_{TsfrFET_n} \right)}$$

- Typically, 2.0 to maintain cell stability.
- Cannot be too stable to write.

Active Pull Down

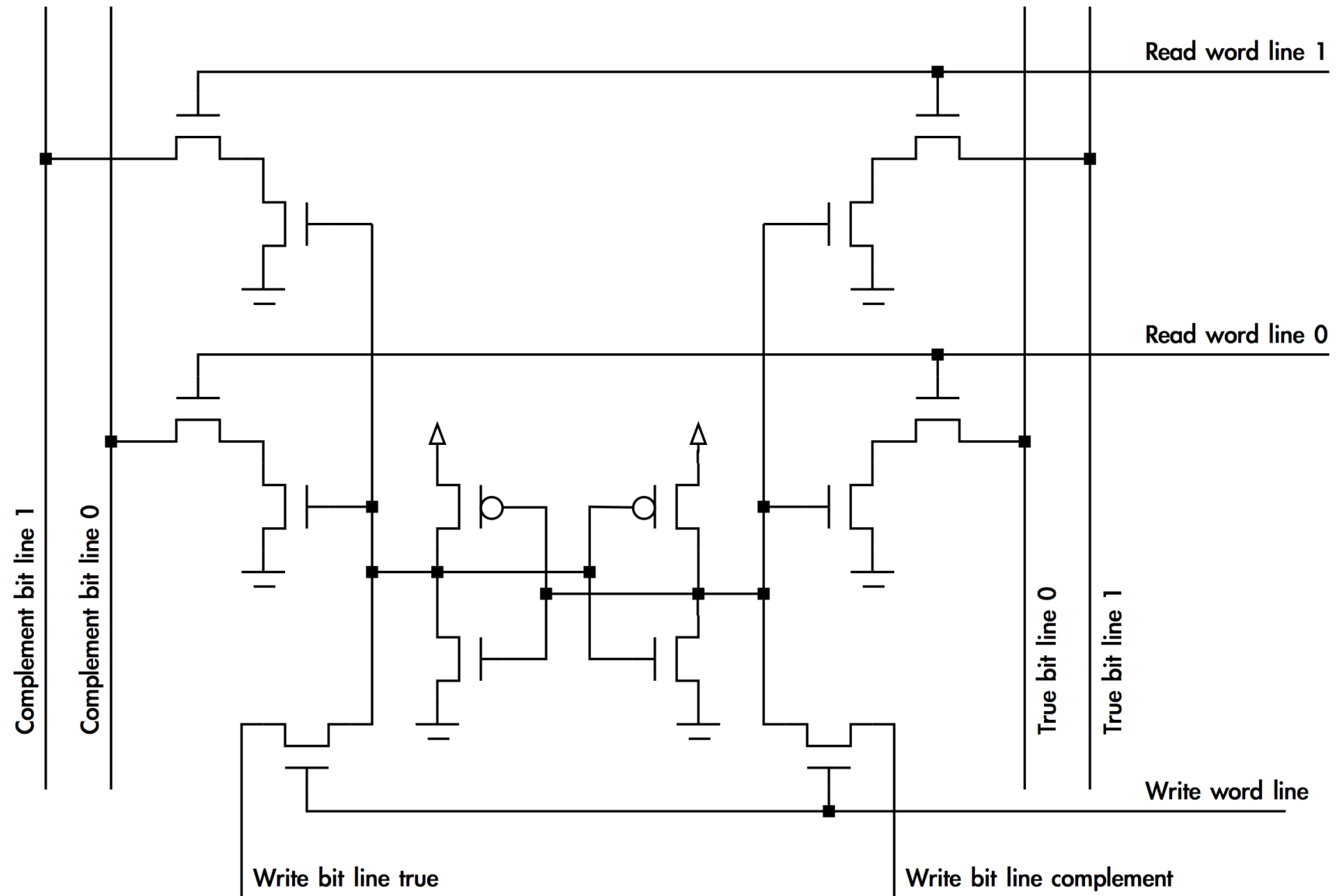

Multi-Port Memories




- Cell basics
- Timing issues
- **Layout considerations**

Capacitive Coupling



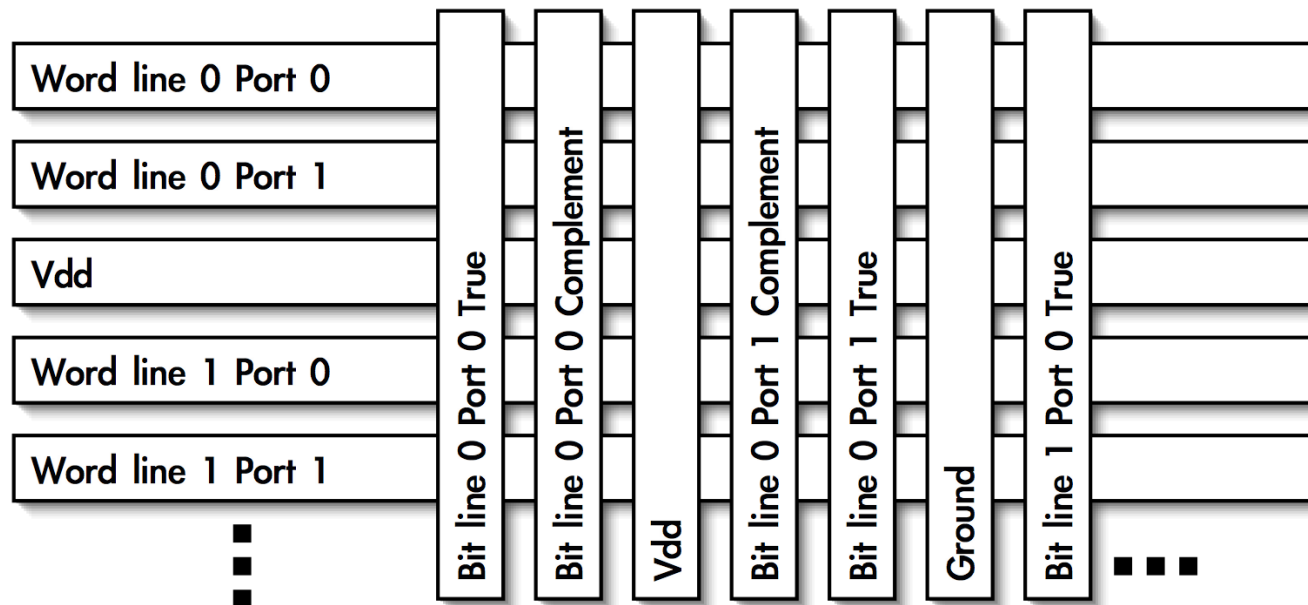- Capacitive coupling between adjacent word or bit lines is a severe problem.
- Shielding needed to prevent excessive coupling into the read bit lines.
 - The read bit line is only held high capacitively.
 - Usually, alternating ground and Vdd lines.



Other Considerations



- A multi-port memory cell is asymmetric.
 - Usually, only stepping is possible.
- Bit line twisting can become very difficult.
 - The coupling concerns must be examined more carefully.
- Redundancy may become a necessity as the multi-port memory size grows.
 - A failure, on any port, must cause complete replacement of the cell with a redundant one.

Summary



- Multi-port memories have many similarities to standard one-port SRAMs.
- The possible interactions between the ports must be carefully analyzed.